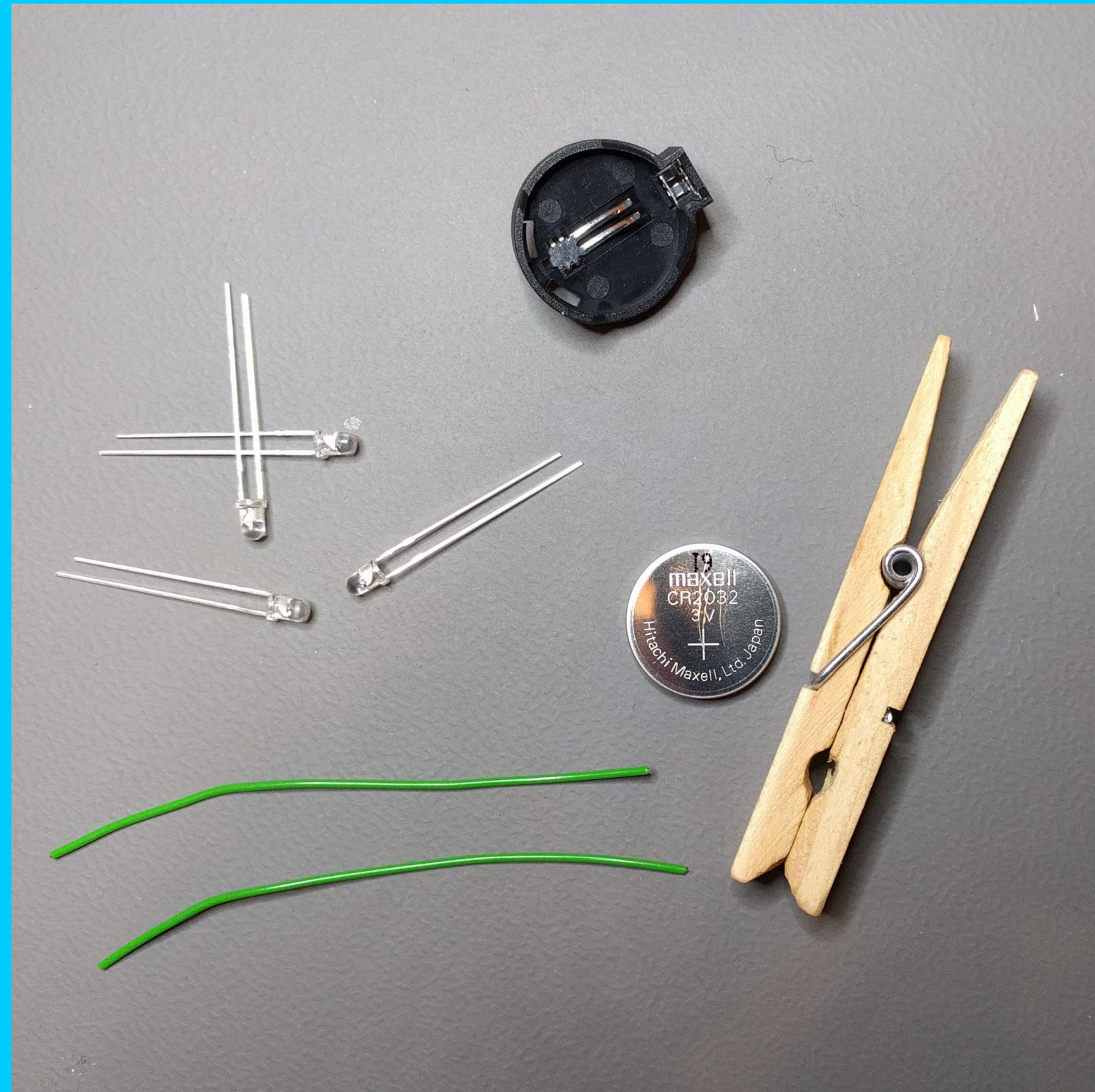


# KLANNMERWAT!

## 1. All You Need




- 4x LEDs
- 1x Battery Holder
- 1x Battery CR2032
- 2x Wires
- 1x Wooden Peg

## 2. Drill Some Holes




- Watch your hair!
- Don't make holes in your finger

## 3. Add Some LEDs

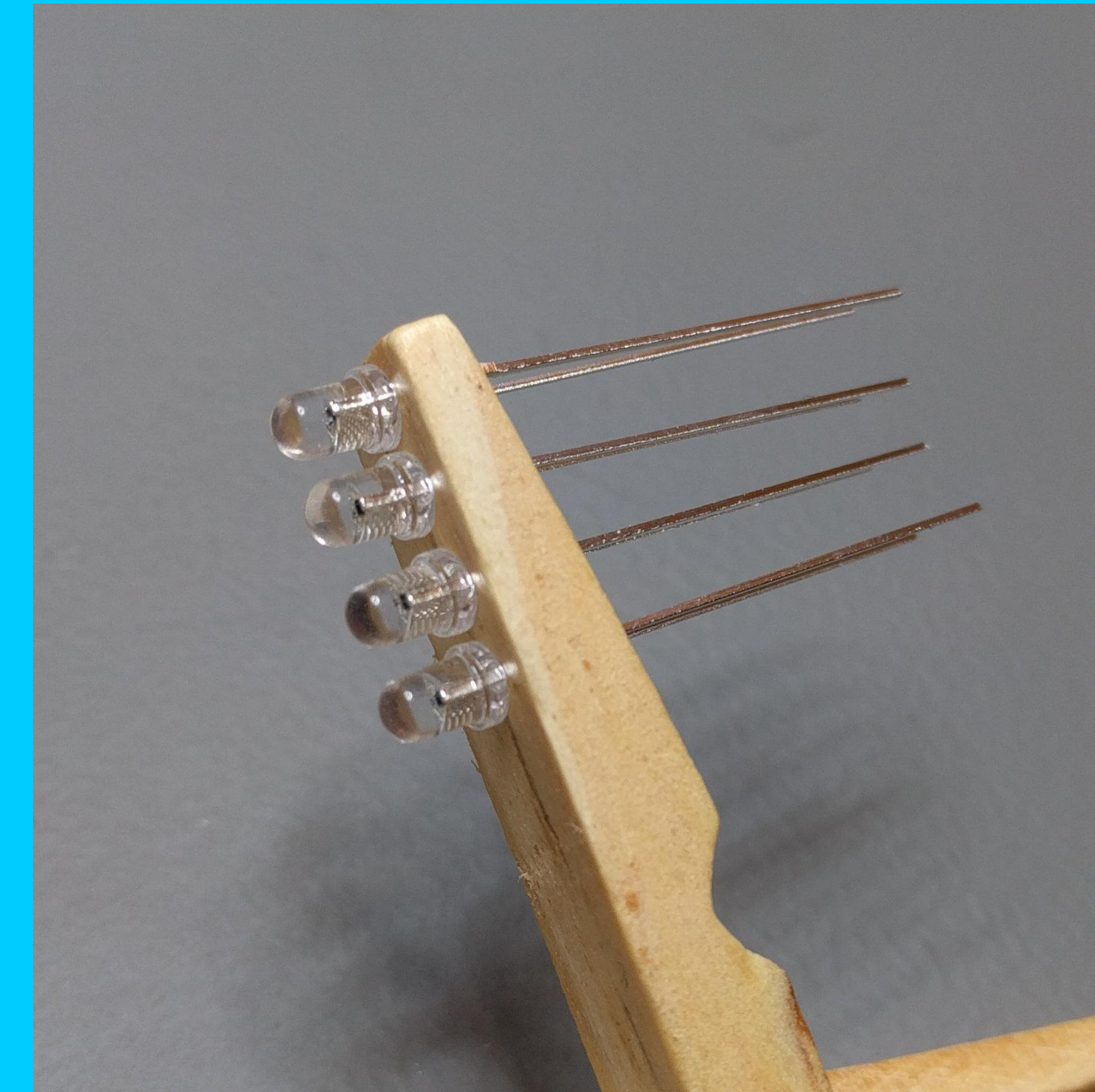


- LEDs have one longer leg
- All long legs must be on the same side!

## 4. Bend all the Tings

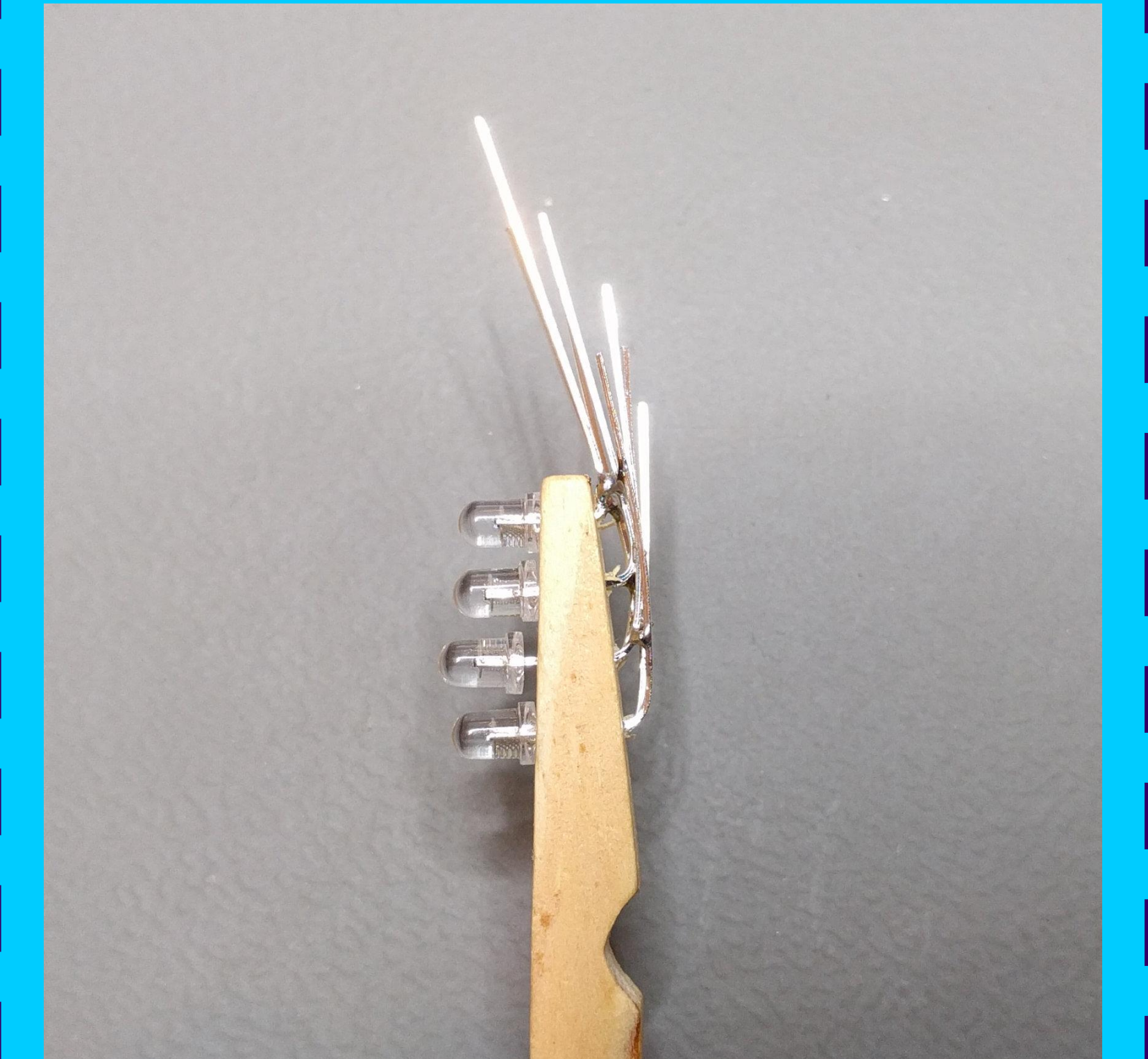

- Bend all Legs
- Connect all long legs
- Connect all short legs
- Long and short legs must not touch!

## 5. Connect Wires

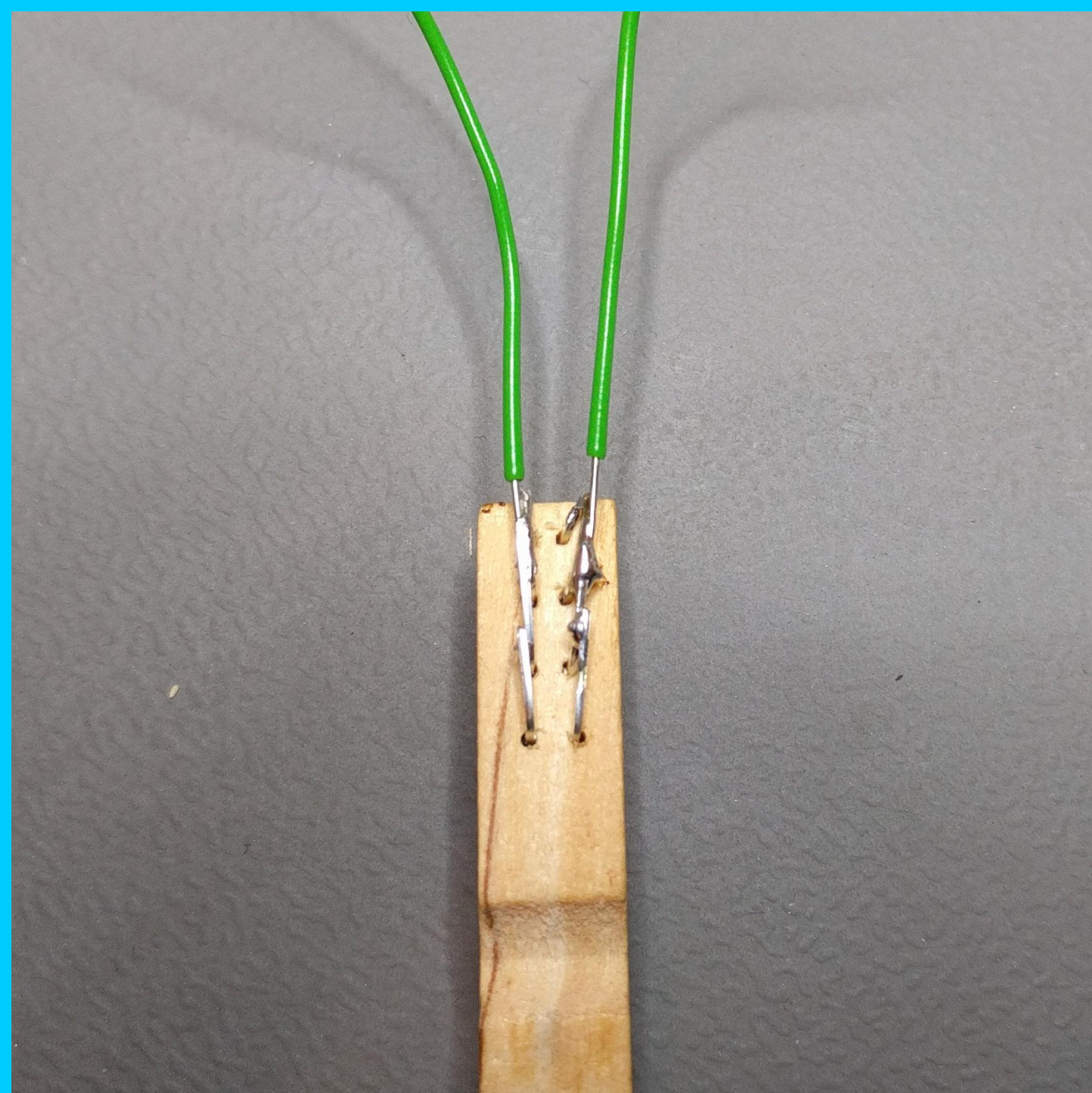


- Clip the legs
- Connect one wire to each leg

## 6. Bend More Things



- Bend the legs of the battery holder to the inside!
- They break if you bend the other way

## 7. Connect Battery

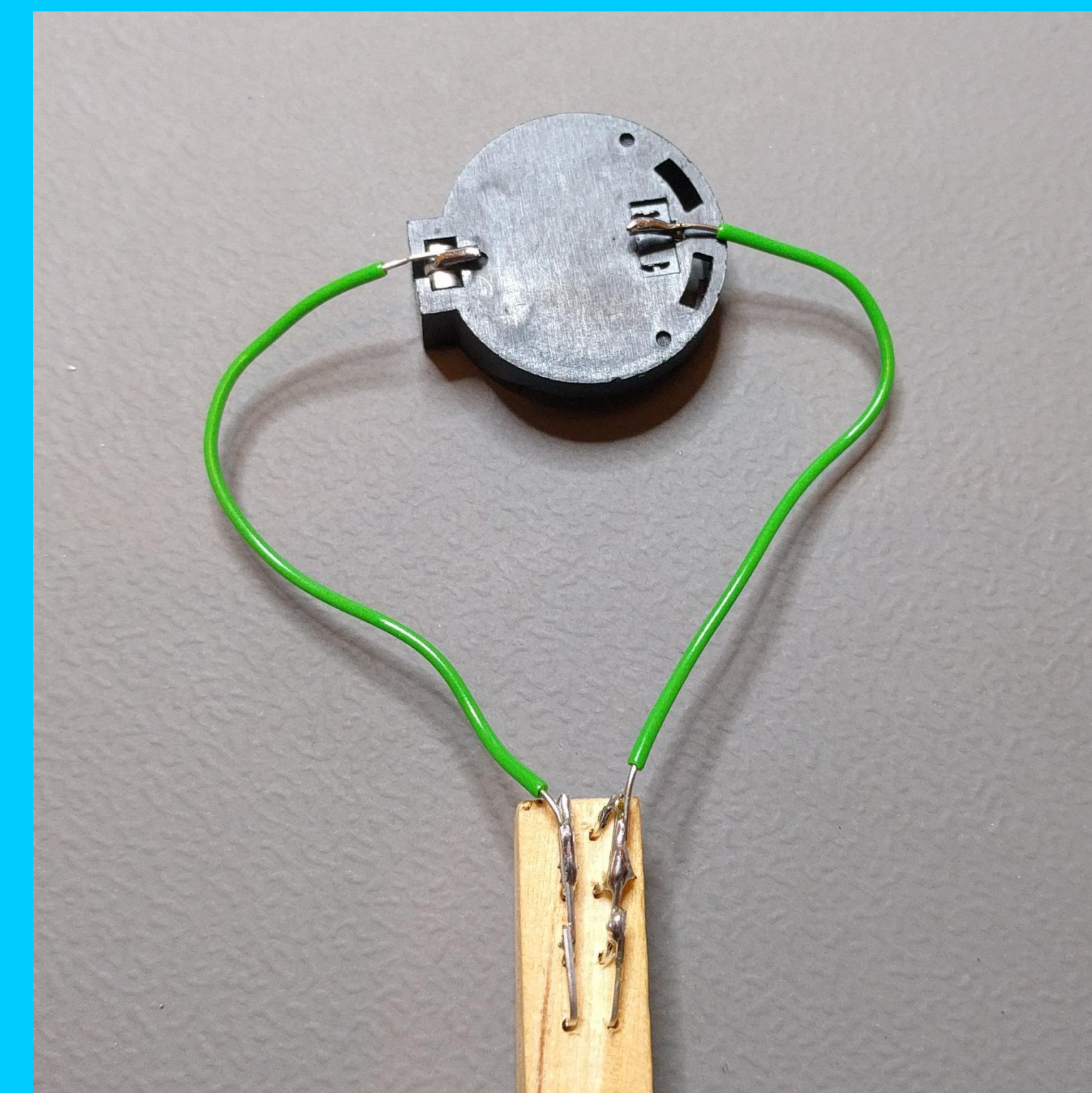

- Insert battery
- Hold wires to the battery holder
- Connect them when the LEDs shine

## 8. Put it Together



- Join together the peg
- Glue battery holder to peg
- Nibble-Peg is finished
- Shine!